

There are a variety of different ways in which the control voltages can be programmed and stored: e.g. via potentiometers, switches, sample-and-hold circuits or digital memories. The method adopted here is to encode the voltage digitally and store it in a RAM. When the contents of the memory are read out, they are fed to a D/A converter, which provides an analogue signal suitable for feeding to the synthesiser VCOs. In addition to the pitch of the notes (i.e. their frequency), their relative length can also be programmed. The duration of each note can be selected in the ratio of 1 : 2 : 4 : 8. The block diagram of the programmable

circuit and the 'subsidiary' address counter, however, even longer (or indeed shorter) sequences are also possible. The note length is controlled by a D/A converter and VCO, the output of which varies the clock frequency of the main address counter. The analogue voltages from output A are fed to the synthesiser VCOs; at output B a gate pulse is generated to accompany each note. The gate pulse, whose width can be varied, is used to determine the start and duration of the envelope control voltage generated by the ADSR module of the synthesiser. The complete circuit diagram of the programmable sequencer is shown in

programmable sequencer


Sequencers are extremely popular add-on units for music synthesisers. They are used to store pre-programmed sequences of control voltages for the synthesiser VCOs/VCFs; the control voltages can be 'played back' into the synthesiser, thereby generating note sequences which can be used for example to provide the backing to a manually played melody.

sequencer is shown in figure 1. The pitch (i.e. its position on the musical scale and its octave) and length of the note are set up in binary code on switches which are connected to the data inputs of the RAM (see figure 3). The address into which the data is stored is determined by an address counter. In actual fact, two address counters are employed, one of which (the 'subsidiary' counter) is clocked by the other ('main' counter). When the stored melody is to be played back, the address counter steps through each of the memory locations in turn. The data is read out and fed to the digital-analogue converters, which provide the actual control voltages for the VCOs. During normal operation the circuit can store 16 sequences of 16 notes apiece, i.e. a combined sequence of 256 notes; with the aid of the reset

figures 2a and 2b. Figure 2a contains the digital section of the sequencer, comprising the memory, address counter and reset circuit, whilst figure 2b shows the D/A converters and output stages. Two 2101's, 256 x 4-bit RAMs, connected in parallel from the memory in which the digitally encoded control voltages are stored. The higher order addresses of the input data are set up on switches S2...S5. The flip-flop (IC11) interposed between the switches and the RAMs ensure that the new address set up on S2...S5 is only presented to the address inputs of the RAMs after the previous note sequence has ended. The main address counter is formed by IC10. The counter is clocked, via IC6, by the analogue section of the circuit shown in figure 2b. This counter generates the 'low order' addresses,


C. Voss

1

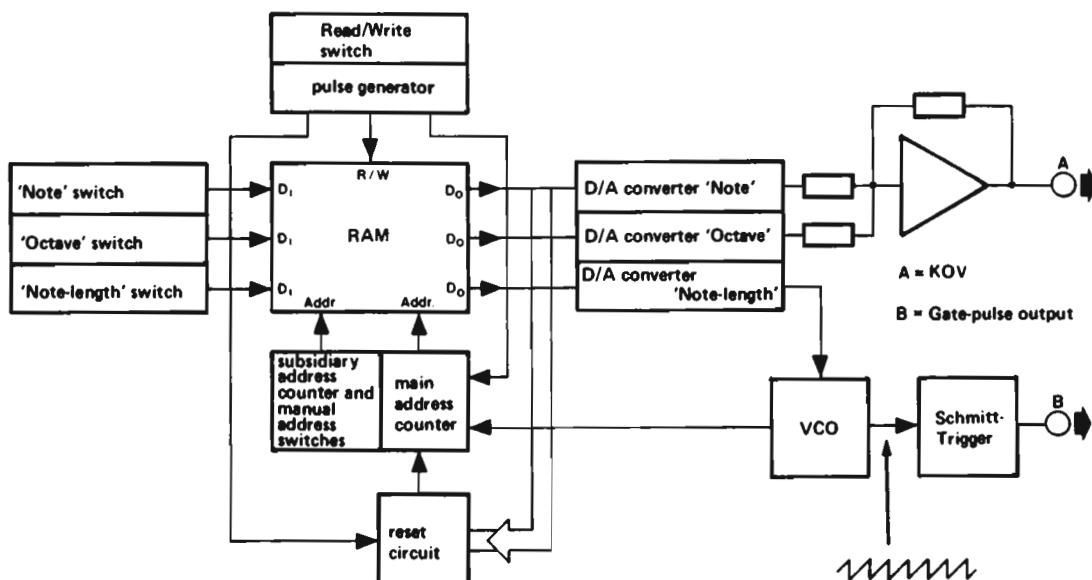

2b

d

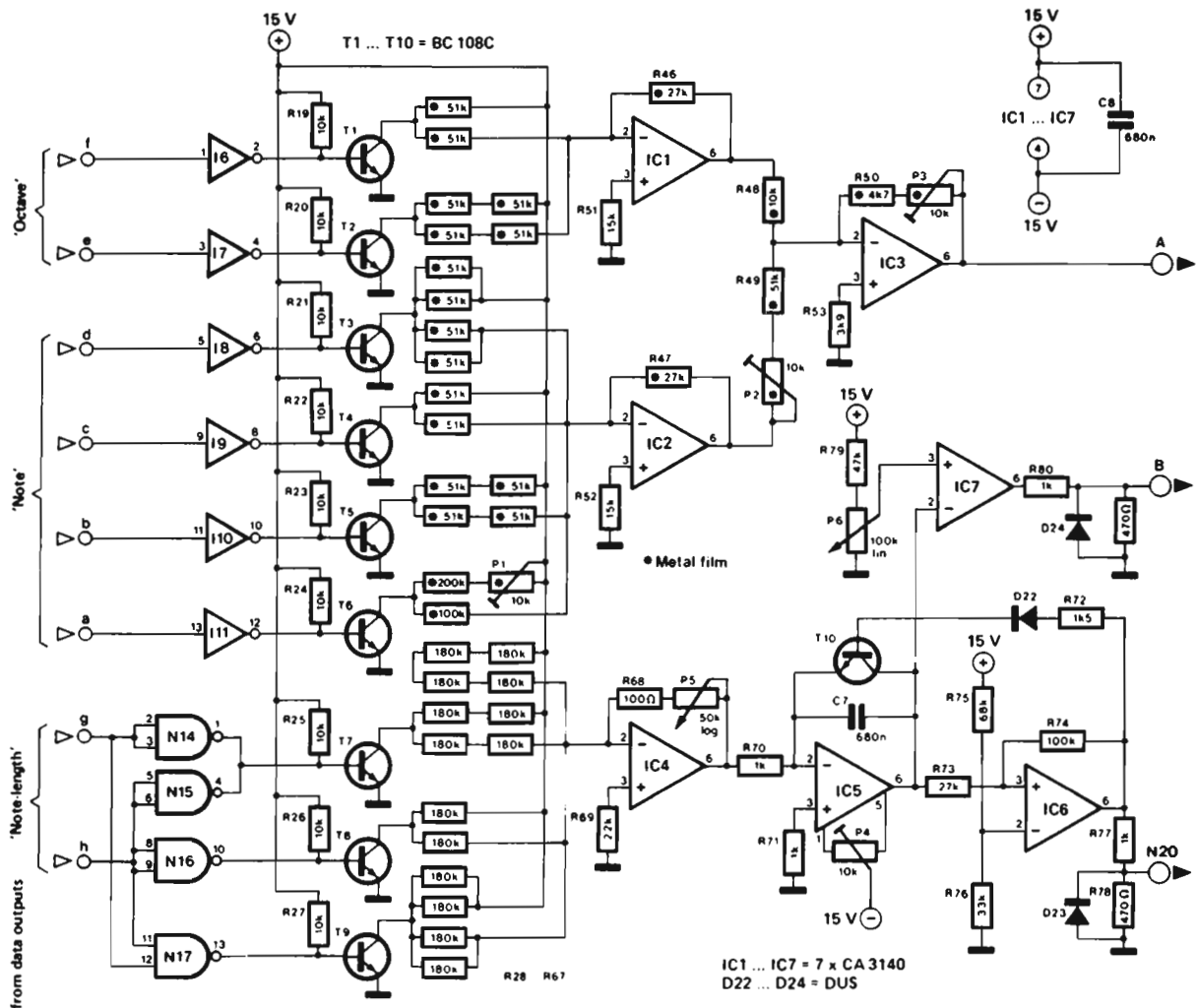


That is to say, when the digital input signal increments by '01', the output voltage doubles. The output of IC4 is fed to a sawtooth generator formed by IC4 and IC5; this both clocks the main address counter (IC10 in fig. 2a) and, via the Schmitt trigger IC7, provides a variable-width gate pulse. In spite of the six adjustment points

(potentiometers P1...P6), the circuit can be set up fairly simply, without the need for any special measuring equipment. The circuit is adjusted correctly when a change in the 'e' input from '0' to '1' causes the voltage at output A to increase by 1V. This voltage can be adjusted by means of P3. P2 should be set such that the output voltage changes by 0.5V when inputs 'b' and 'c' go high.

Fine tuning is performed by means of P1. A change in state of input 'a' should correspond to a change of 1/12V in the output signal. P5 should be adjusted such that the output frequency doubles when input 'g' goes high. P4 is used to compensate the offset voltages of IC4 and IC5. Finally, P6 determines the width of the gate pulse.

3

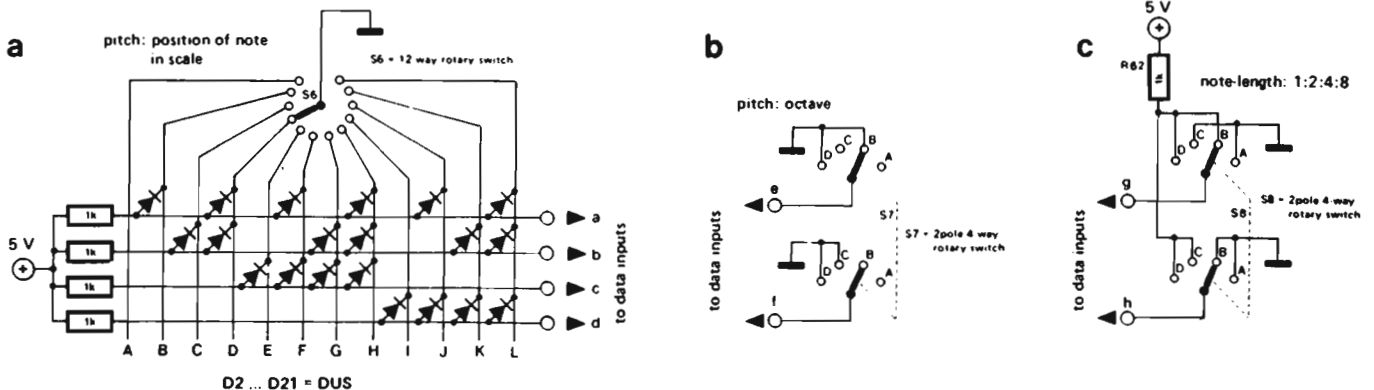

D2...D21 = DUS