

Voltage-Controlled Clock for Analogue Sequencers



by Dr. W.J. Phillips

This article describes the construction and design of a voltage controlled clock which outputs a train of square waves at standard TTL level. It was designed to fulfil a need for my particular system which includes three Powertran 1024 digital sequencers, two

custom-built analogue sequencers, custom-built patch-board, programmable percussion machine and recently an Amdek programmable rhythm generator. However, there's no reason why the unit shouldn't work perfectly in other systems.


When performing live or in a studio it is convenient to be able to have sequencers and percussion generators running together in synchronisation. It is also convenient to be able to change the speed at which the units are clocked quickly and easily, preferably with a bank of presets. Accordingly it was decided to use a Voltage Controlled Oscillator as the heart of the circuit and the CEM3340 IC was chosen for this purpose. It's not the cheapest available but if the correct high stability components are used in the frequency-determined circuitry it is very stable and very reliable. If it's good enough for Sequential Circuits to use I felt it was good enough for me!

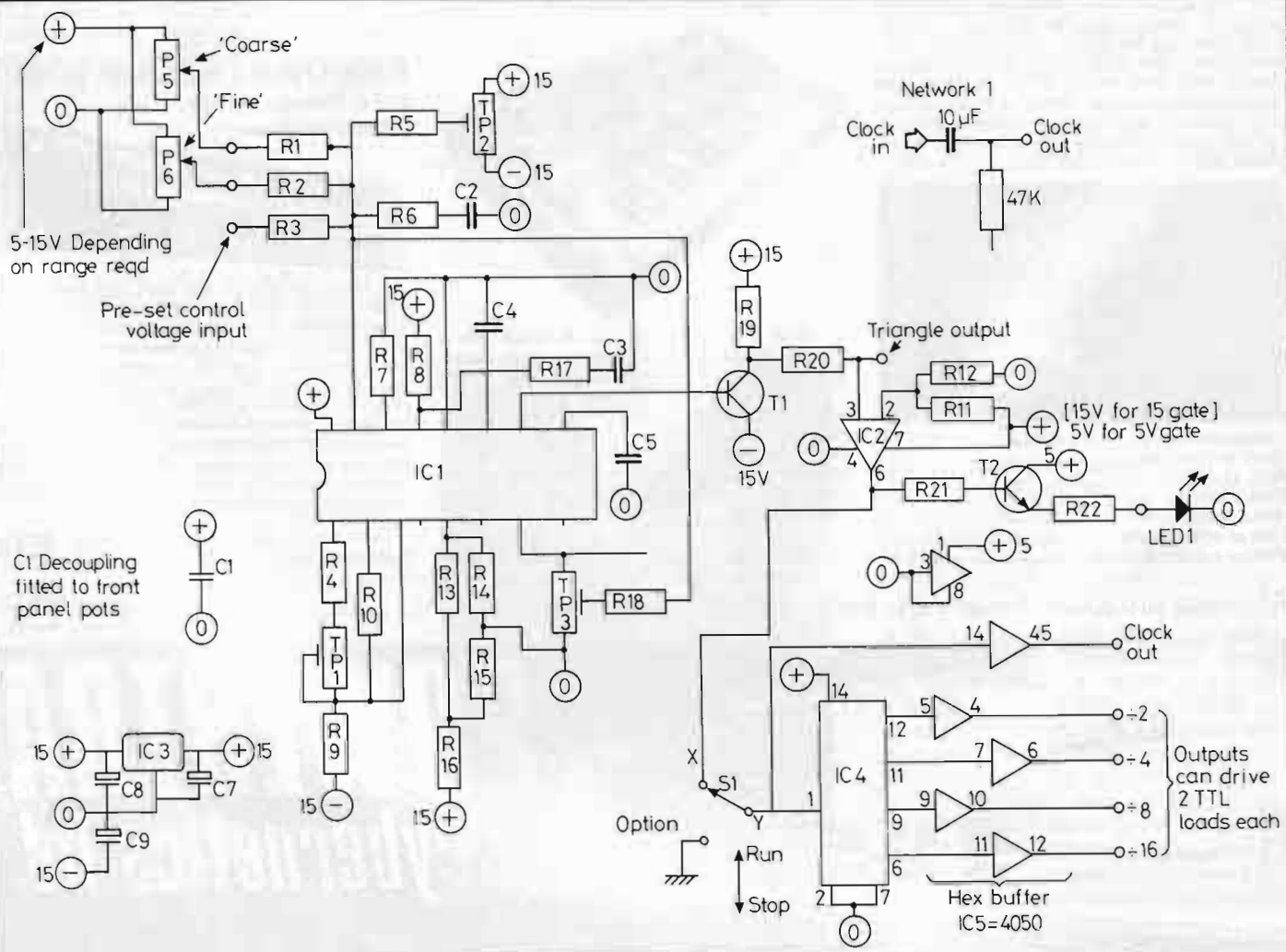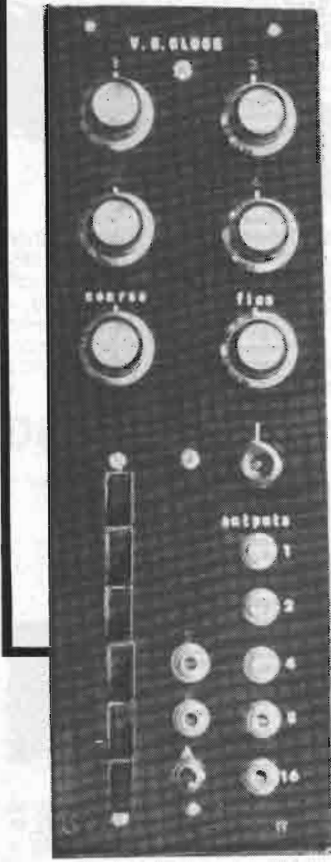Since it's useful to have different modules running at different speeds, the VCO is followed by a divider circuit which divides the basic clock plus down by five stages. The outputs are buffered and each output can drive two standard TTL loads. The unit was originally configured on a 9" x 3" panel so that it could be incorporated within the scheme of the standard Digisound 'system 80' synth-



Foil pattern

voltage controlled clock

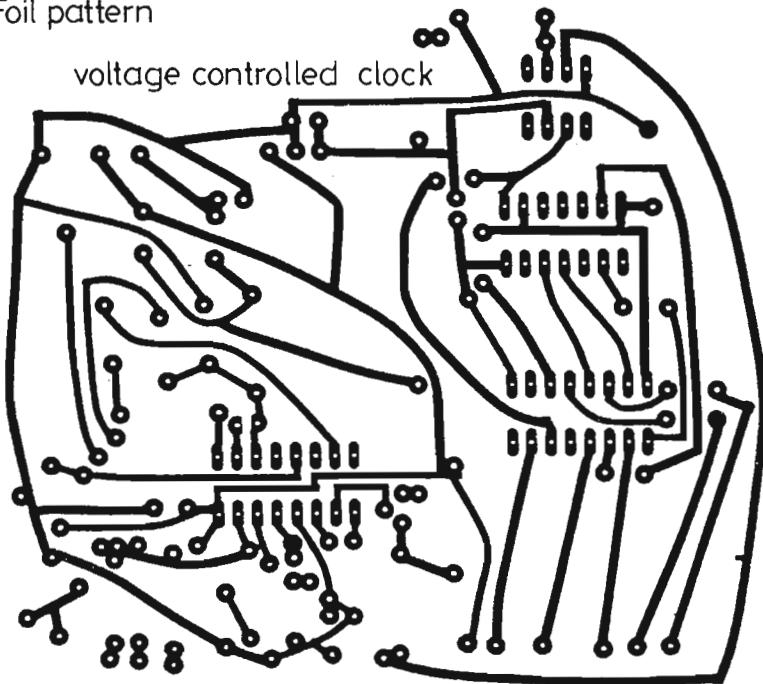


esiser. The Curtis chip produces square waves, triangles and sawtooths as standard and therefore when not being used as a voltage control clock this unit can be used as a voltage controlled low frequency oscillator.

Circuit Description

The heart of the unit is the CEM3340 voltage controlled oscillator. To understand how this works fully, the best thing to do is to get a CEM3340 data sheet from those awfully nice Digisound people. The frequency control voltage is injected into pin 15. The design allows for coarse and fine controls and also a preset mounted on the board, namely TP2 which sets the initial frequency with no other control voltage applied. Preset control voltages via R3 come from a variety of sources; in the prototype four 100K linear pots were mounted on the front panel and two jack sockets were provided for external control voltages. These were then selected by a six-way interlocking switch bank. A cheaper alternative would be to use a six-way rotary switch.

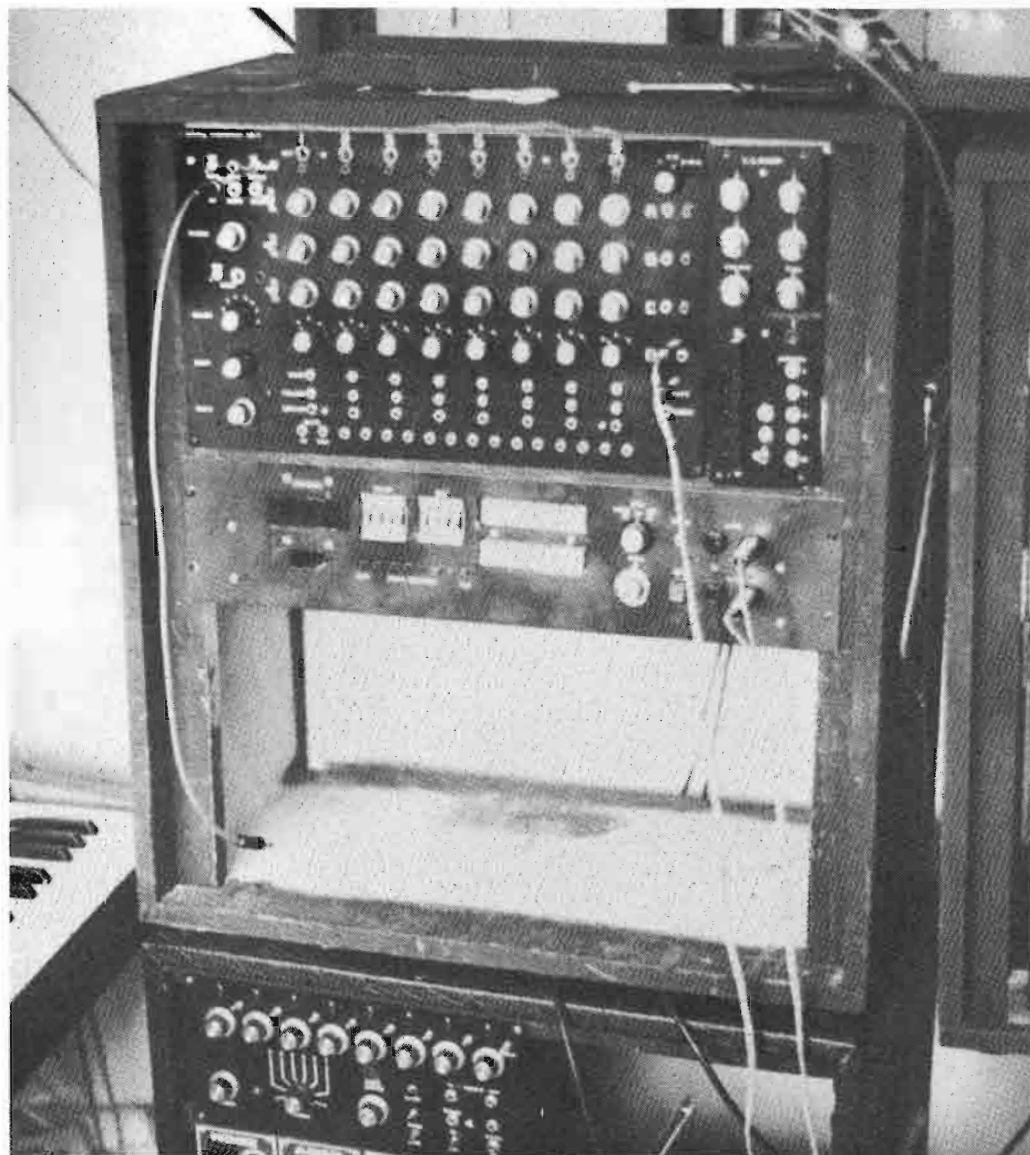The facility to inject external control voltages means that the frequency of the clock can be controlled from a one octave per volt synthesiser keyboard or from



The VC Clock (top right) located within the author's modular synth rack.

